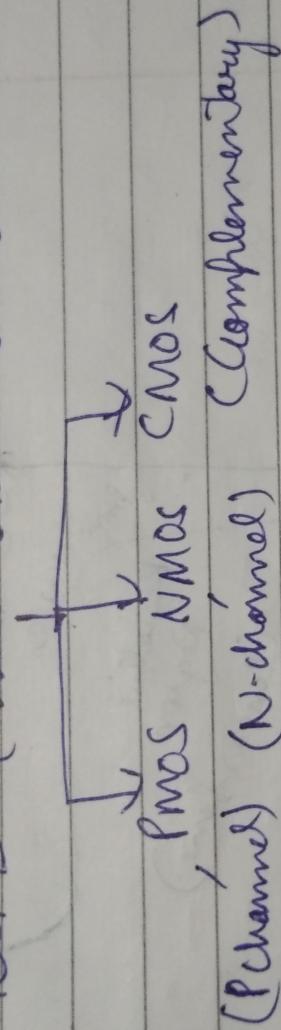


$$R_c = 0.5 \text{ k}\Omega$$


④ FET (Field Effect Transistor):-

Crack (G<sub>r</sub>)  
Source (S)  
Drain (D)

JFET (Junction FET)  
MOSFET (Metal Oxide Semiconductor FET)




Current gain ( $\alpha$ ) ( $\beta$ )

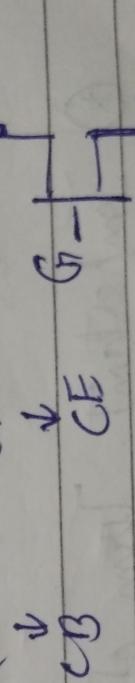

Voltage gain


④ BJT (Bipolar) Current control, current gain  
FET (Unipolar) Voltage cont. & voltage variable  
Voltage Regulator.

Date: / /

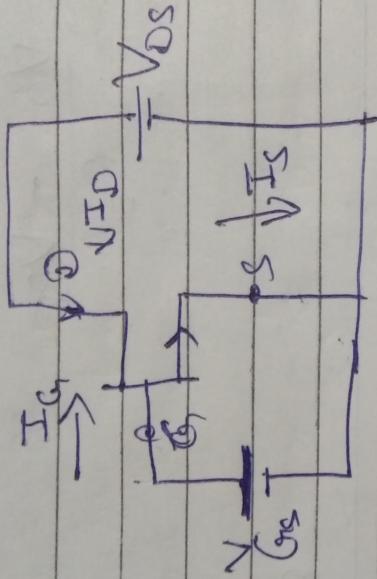

Pinch off  $\rightarrow$  is condition when channel formed.


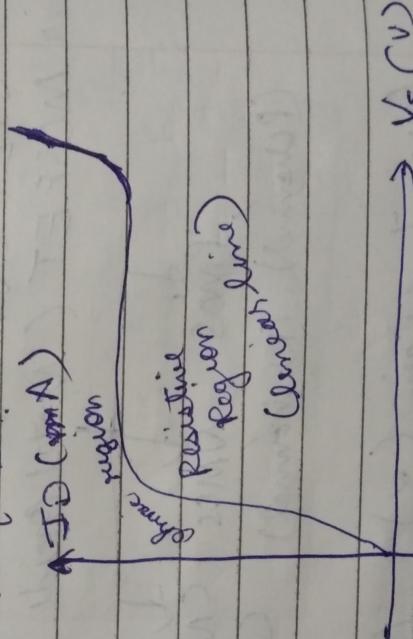
Threshold Voltage: minimum amount of voltage required for conduction to start in FET.



\* Important Term of JFET :-



- ①  $I_{DSS}$  = Short gate drain current.
- ②  $V_p$  (Pinch off voltage)
- ③ Gate source cut off voltage  $V_{GS}(off)$

$$\frac{V_{GS}}{-V_{GS}}$$

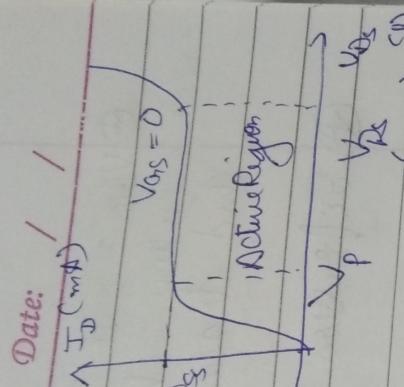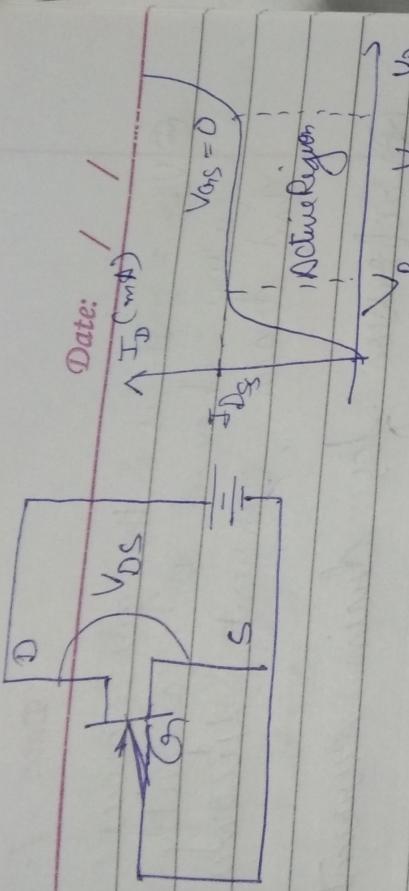

★ It is a drain current with source short circuit to gate ( $V_{GS} = 0$ ) &  $V_{DS}$  finite voltage, sometimes its called zero biased current.

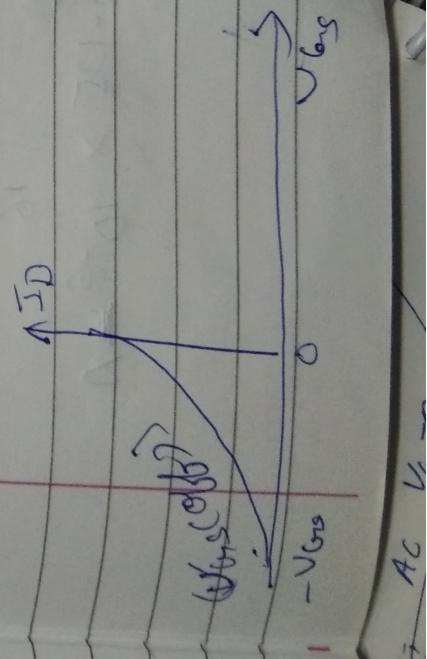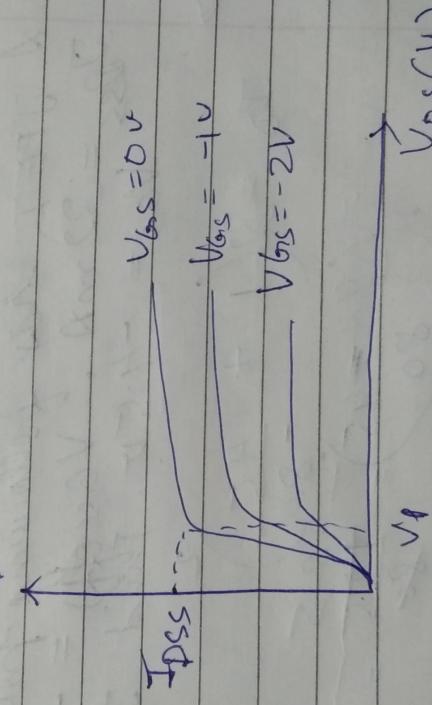② Punch off  $\Rightarrow$  It is defined as the min current  $I_D$  at which  $V_{GS} = 0$  essentially becomes constant.



$V_{DS}$

AC

Date: / /

④  $V_{GS} =$  It is the gate source voltage where channel is completely cut off and drain current becomes zero.

⑤ Expression for drain current for JFET

$$I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_{GS(\text{off})}} \right]^2$$

$I_D$  = drain current at given  $V_{GS}$

$I_{DSS}$  = shorted gate drain current

$V_{GS}$  = gate source voltage

$V_{GS(\text{off})}$  = gate source cut off voltage

Q → A JFET has following parameter

$$I_{DSS} = 32 \text{ mA}, V_{GS(\text{off})} = -8 \text{ V}$$

$$V_{GS} = -4.5 \text{ V}$$
 Find  $I_D$ .

$$\begin{aligned} I_D &= 32 \left( 1 + \frac{-4.5}{-8} \right)^2 \\ &= \left( \frac{80 - 45}{80} \right)^2 = \frac{125}{80} = \frac{25}{16} \times 32 \\ &= 6.125 \times 10^{-3} \text{ A} \end{aligned}$$

=

Ques → Is JFET to be used as an amplifier having following para.


$$I_{DSS} = 20 \text{ mA}$$

Plot trans-conductance curve.

Assume  $I_D = 1 \text{ mA}$

$$I_D = 20 \times 10^{-3} \left[ 1 + \frac{V_{GS}}{25} \right]^2$$
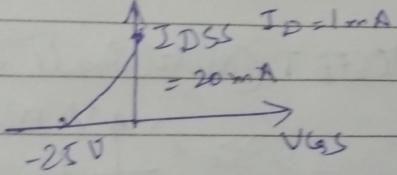
$$\left( \sqrt{\frac{1}{20}} - 1 \right) 25 = V_{GS} = -19.4 \text{ V}$$



Ans → Is JFET has drain current of  $5 \text{ mA}$ ?

If  $I_{DSS} = 10 \text{ mA}$ ,  $V_{GS(off)} = -6 \text{ V}$ . Find value of ①  $V_{GS}$ , ②  $V_P$ , ③ Plot curve.

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$


$$5 \times 10^{-3} = 10 \times 10^{-3} \left( 1 + \frac{V_{GS}}{6} \right)^2$$

$$V_{GS} = -1.76 \left( \sqrt{\frac{1}{2}} - 1 \right)^6$$


$$= -1.76 \text{ V.}$$

$$V_P = -V_{GS(off)}$$



$$= 6 \text{ V.}$$

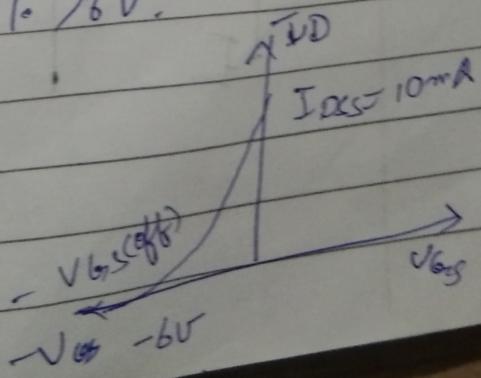

Date: / /

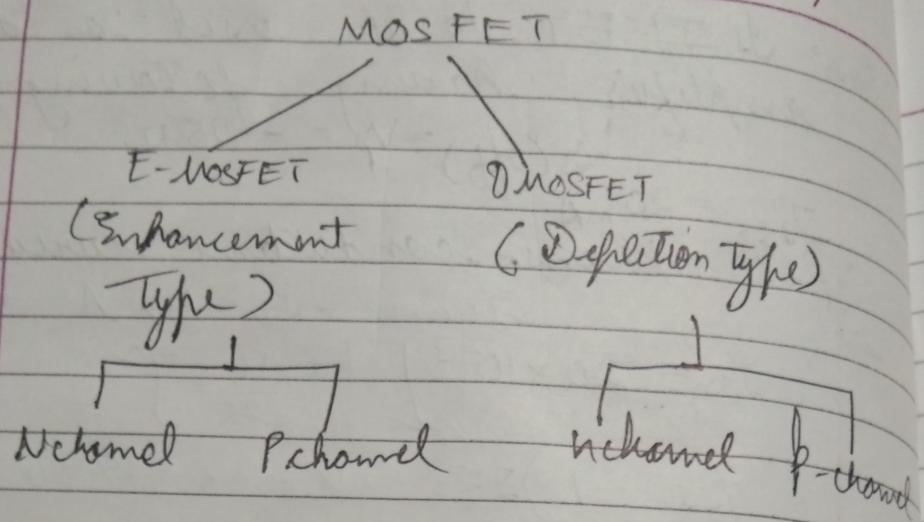

MOSFET (Metal Oxide Semiconductor FET)

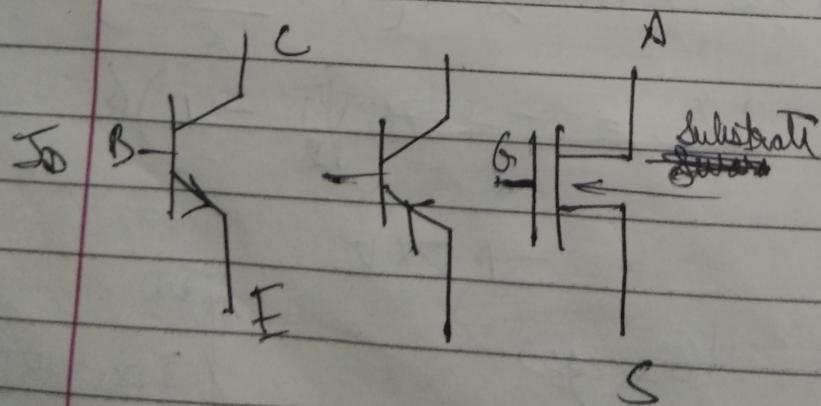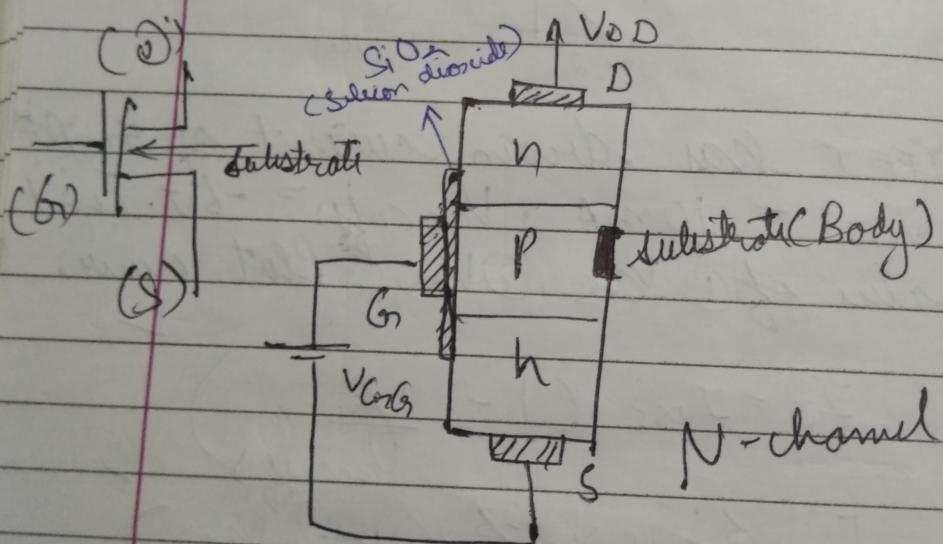

## JFET


Junction Field Effect Transistor

Date: / /

## MOSFET

Metal Oxide Semiconductor field effect Transistor

- ② 3 terminal Gate, Source, drain.

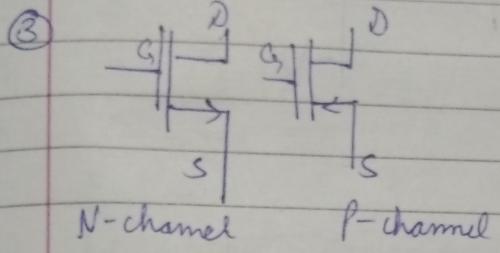

- ③ Extremely high Input Impedance


- ④ Biasing method - Self Bias

Voltage divider bias  
gate bias

- ⑤ Bias instability.

- ⑥ Works in depletion mode only.

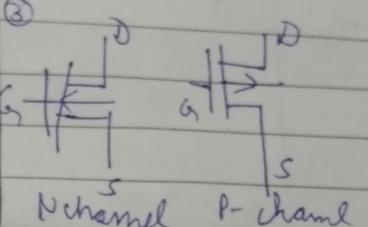- ② 4-terminal Gate, Source, drain, substrate



- ④ high input impedance w.r.t. JFET

- ⑤ Biasing method -

Self Bias


Voltage divider Bias

Zero Bias

Cross Bias

Bias Instability

- ⑥ Works in enhancement mode.

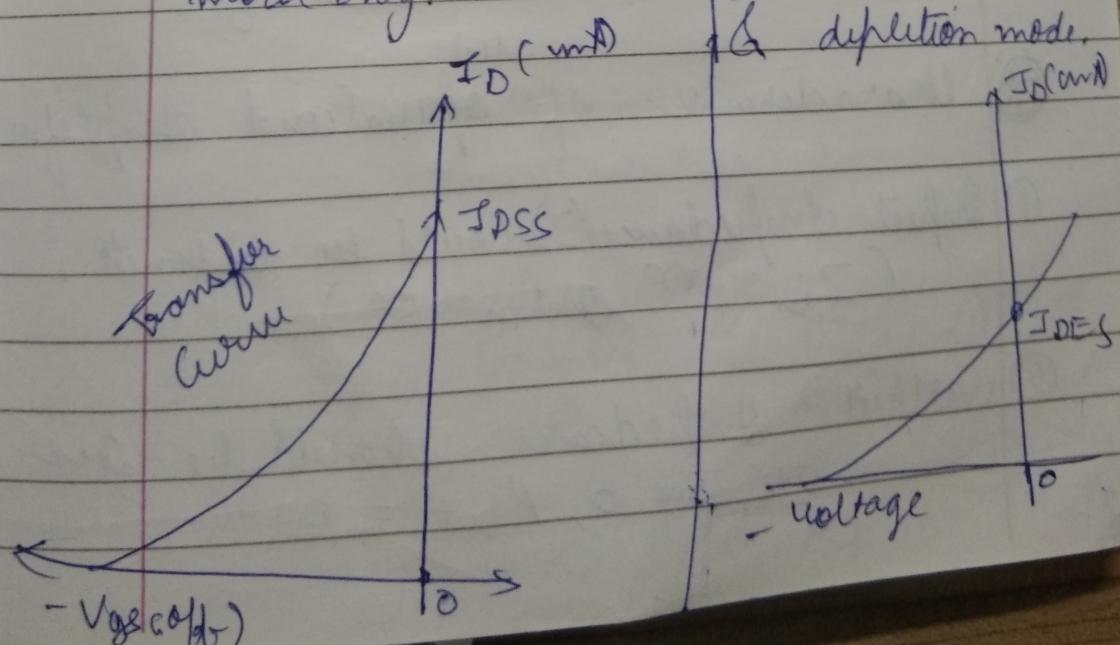



Ch →

Date: / /

## ★ Operational Amplifier (Op-amps)

Inverting

Non Inverting  
Terminal

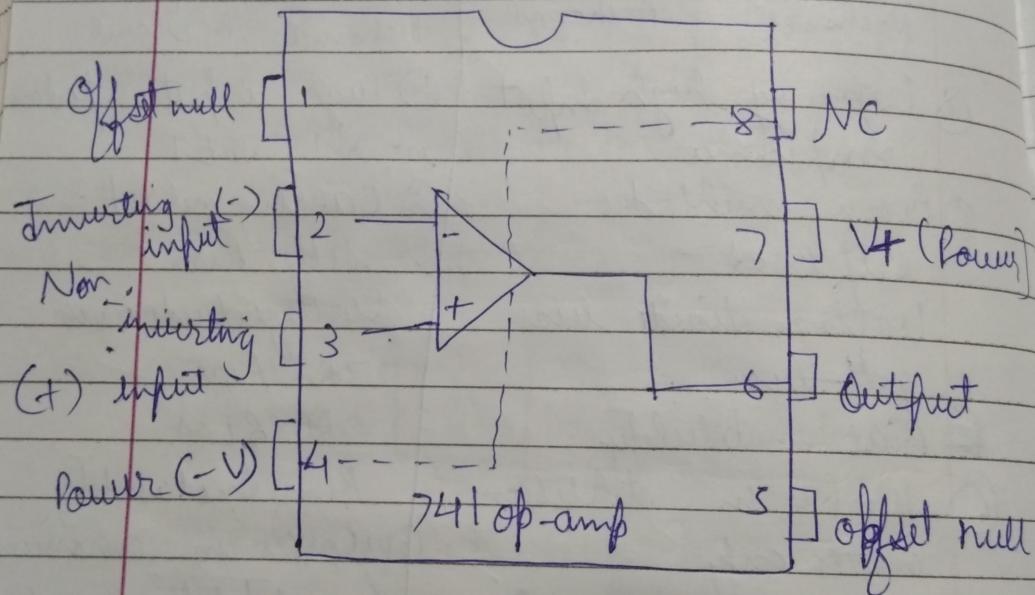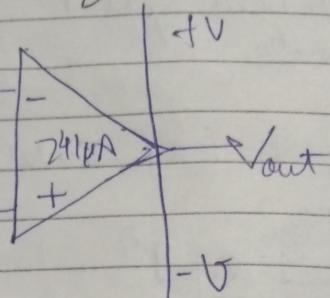

## ★ Ideal characteristic of operational amplifiers

① Input Impedance ( $Z_{in}$ ) should be infinite.  
( $Z_{in} = \infty$  or  $R_{in} = \infty$ )

② Output Impedance should be zero  
 $Z_{out} = 0, R_{out} = \infty$

Date: / /

③ Open loop gain should be infinite.

$$G = \frac{V_{out}}{V_{in}} = \infty$$

④ Input offset voltage should be 0.

⑤ Noise should be zero.

⑥ Infinite bandwidth.

⑦ Low noise.


⑧ CMRR (Common Mode Rejection Ratio)

⑨ 0 phase shift

⑩ Infinite power supply rejection ratio.

⑪ Input current for input impedance.

### ⑫ Op-amp Inverting Amplifier:

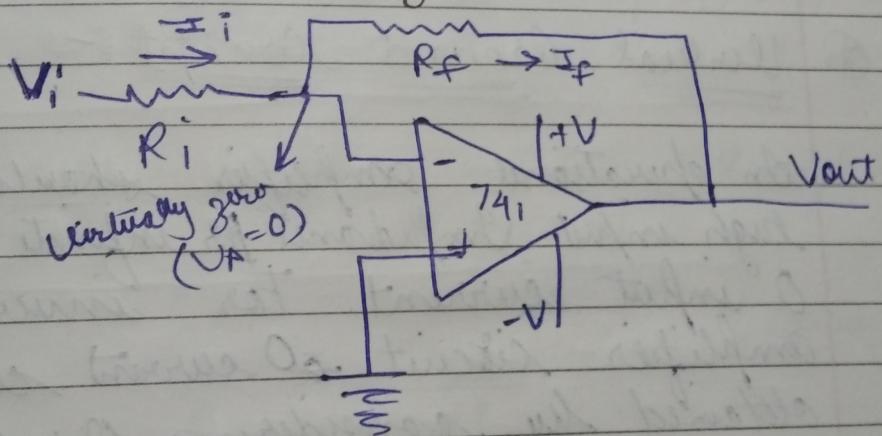

$R_i$  = input resistance

$R_f$  = feedback resistance

$V_i$  = i/p voltage

$V_{out}$  = output voltage.

$$I_i = \frac{V_i - V_A}{R_i} = \frac{V_i}{R_i} \quad \text{---(1)}$$

$$I_f = \frac{V_A - V_{out}}{R_f} = \frac{-V_{out}}{R_f} \quad \text{---(2)}$$

Date: / /

from Q & D  
apply KCL

$$I_i = I_f$$

$$\frac{V_i}{R_i} = -\frac{V_{out}}{R_f}$$


$$\frac{V_{out}}{V_{in}} = \frac{-R_f}{R_i}$$

$$A_{CL} = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_i}$$

Close loop voltage gain
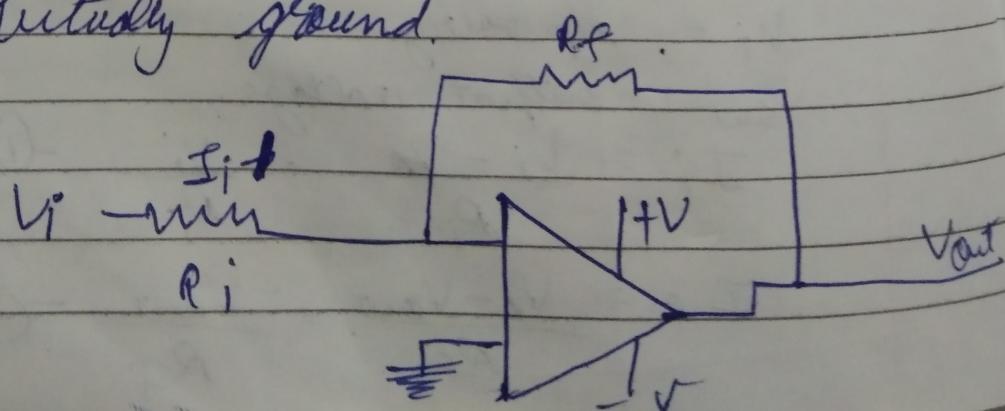
### ① Virtual Ground Concept :-


An operational amplifier should have high input impedance or infinite, and 0 input current. For inverting amplifier circuit 0 current can be obtained by considering 0 voltage from feedback point w.r.t. the ground or this point is called virtually ground.



Date: / /

In circuit of non-inverting amplifier  
 $V_s$  is having zero voltage, that is  
 called virtual & non-grounded but  
 considered) voltage.

### ① Op-amp non-inverting amplifier:-

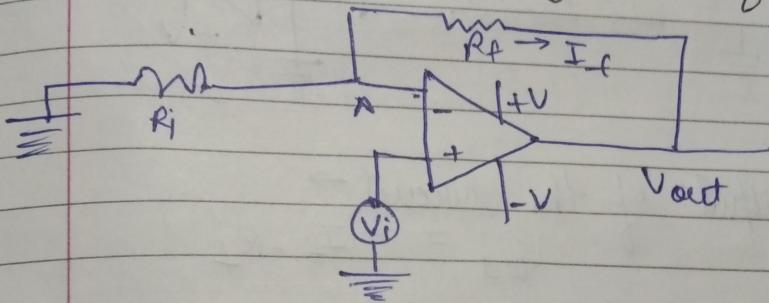

$$\text{Voltage across } R_i = V_i - 0 = V_i$$

$$\text{Voltage across } R_f = V_{\text{out}} - V_i$$

I have  
 and  
 using  
 in the  
 stage

$$\text{Current by } R_i = \text{Current through } R_f$$

$$\frac{V_i}{R_i} = \frac{V_{\text{out}} - V_i}{R_f} \quad [\text{Divide by } V_i]$$

$$\frac{1}{R_i} = \frac{V_{\text{out}} - V_i}{V_i R_f}$$


$$\frac{R_f}{R_i} + 1 = \frac{V_{\text{out}}}{V_i} = \text{Acl}$$

Vout

Date: / /

## ② Applications of Op-amp :-

### i) Adder/Summer amplifier:-

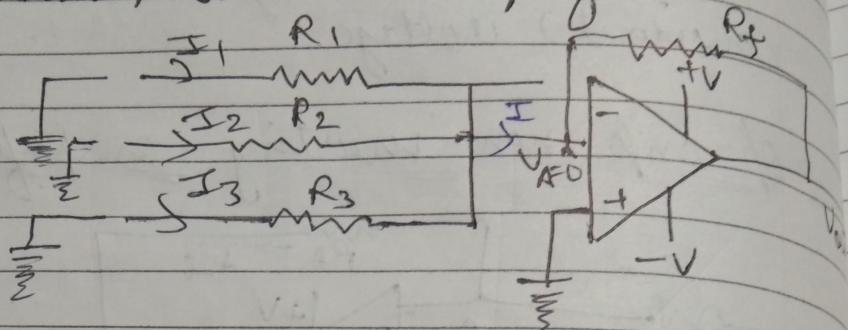

Output of the circuit →

$$V_{\text{out}} = -I_f \cdot R_f$$

$$I_f = I = I_1 + I_2 + I_3$$

$$V_{\text{out}} = -(I_1 + I_2 + I_3) R_f$$

$$\therefore V_{\text{out}} = -R_f \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

Let us assume

$$R_1 = R_2 = R_3 = R$$

$$V_{\text{out}} = -\frac{R_f}{R} (V_1 + V_2 + V_3)$$


Ques → What will be output expression for op-amp if treated as summing amplifier &  $R_1 = R_2 = R_3 = 3K\Omega$ ,  $R_f = 1K\Omega$   
Design circuit?

Date: / /

$$\rightarrow \text{as } V_{\text{out}} = \frac{R_f}{R} (V_1 + V_2 + V_3)$$


$$= \frac{1}{3} (V_1 + V_2 + V_3)$$

Average amplifier:-

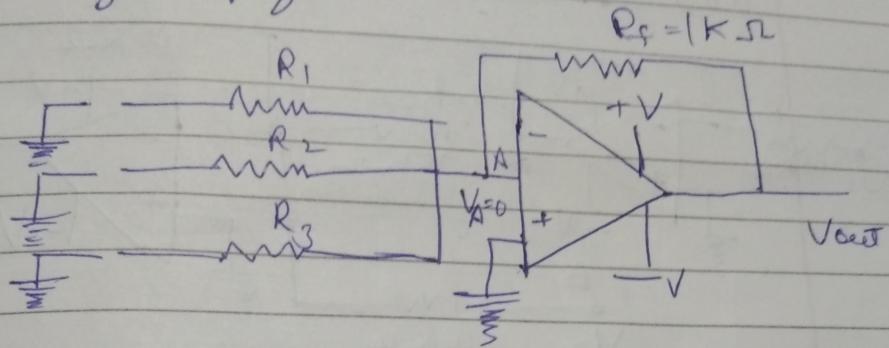

Q → Design a circuit which provides following output  $V_{\text{out}} = + (6V_1 + 2V_2 + 4V_3)$

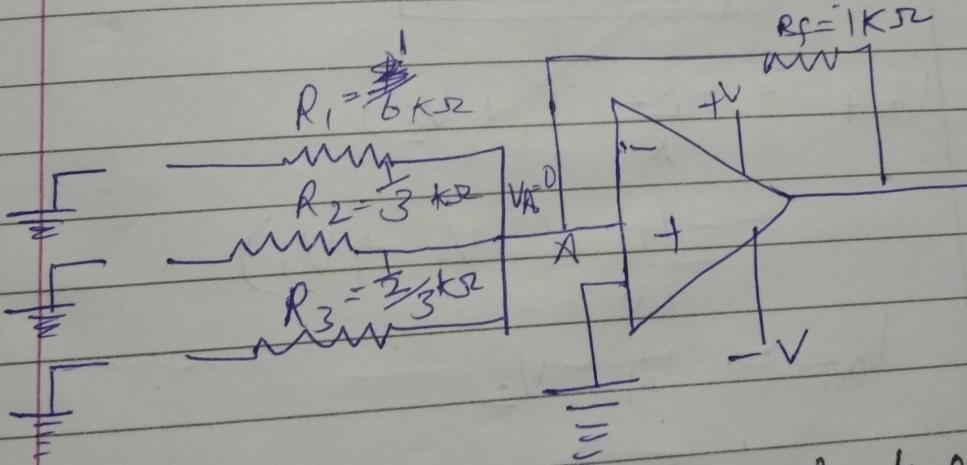
$$V_{\text{out}} = +6 \left( \frac{V_1}{6} + \frac{V_2}{3} + \frac{V_3}{3/2} \right)$$



Q → Design an operational amp. to obtain  
exp: ?  $V_{\text{out}} = (2A + 3B + V_c)$

Date: / /

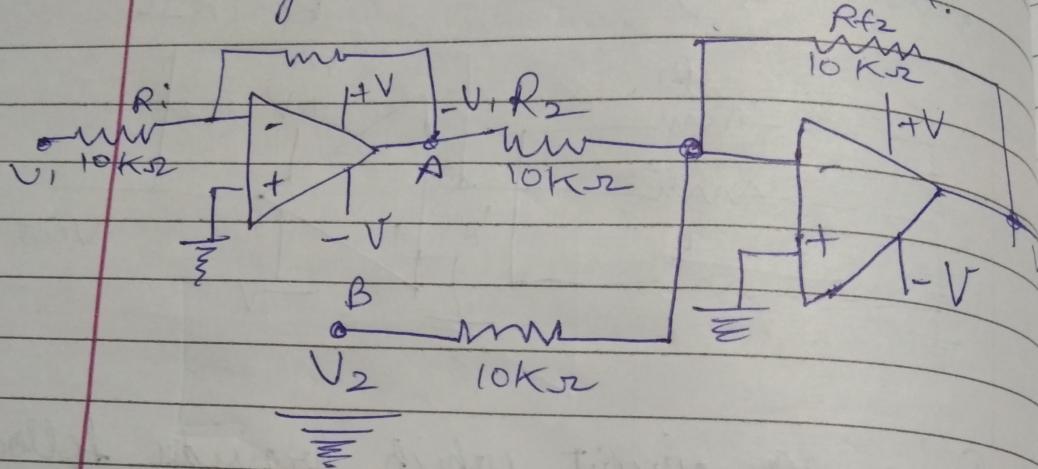2. As subtractor = 1 summing amplifier can be used to provide output voltage in circuit = to diff. of voltages. Such as Subtractor.




$$\frac{V_A}{V_1} = \frac{-R_f}{R_i} = \frac{-10}{10}$$


$$V_{out} = -V_1$$

$$V_{out} = -\frac{R_f}{R}(V_1 + V_2)$$

$$= -\frac{10}{10}(-V_1 + V_2)$$


$$V_{out} = V_1 - V_2$$

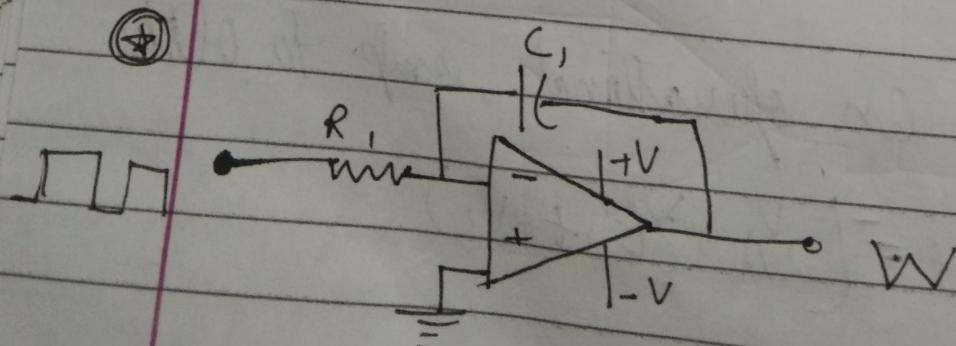

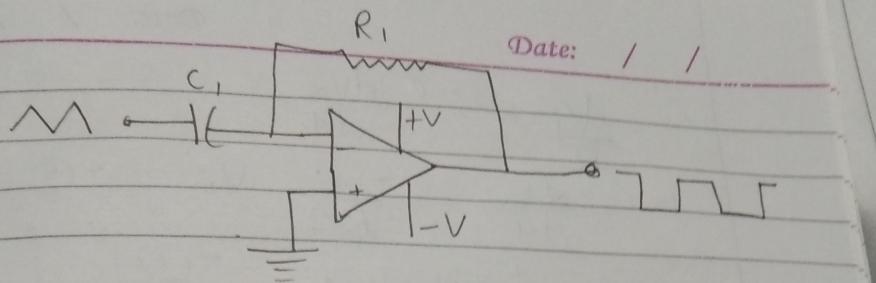

op-amp differentiator

④ Integrator Derivation :-

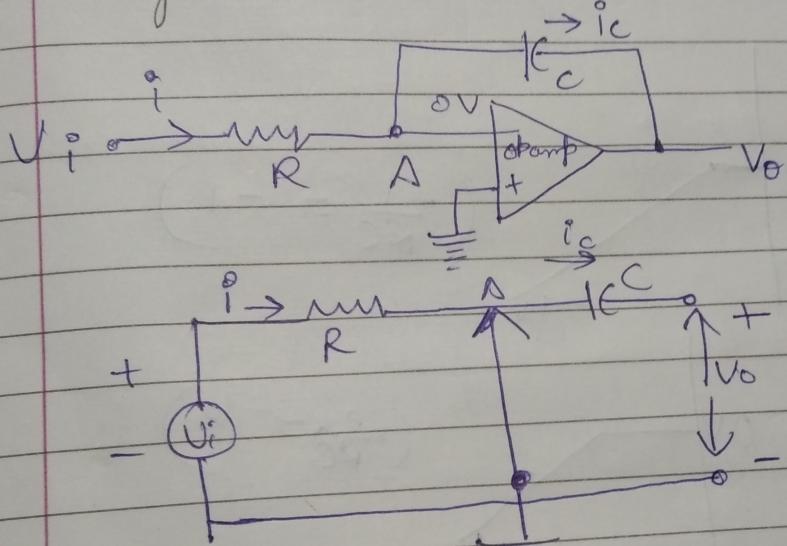

$$\text{At } A: i = \frac{V_i - 0}{R}$$

$$= \frac{V_i}{R}$$

$$V_c = 0 - V_o = -V_o$$

$$i_c = C \frac{dV_c}{dt} = -C \frac{dV_o}{dt}$$

Applying Kirhoff's law  
 $i = i_c$




Date: / /

$$\frac{V_i}{R} = -C \frac{dV_o}{dt}$$


$$\frac{dV_o}{dt} = -\frac{1}{RC} V_i \quad \text{---(1)}$$


Integrating ---(2)

$$V_o = -\frac{1}{RC} \int_0^t V_i dt$$

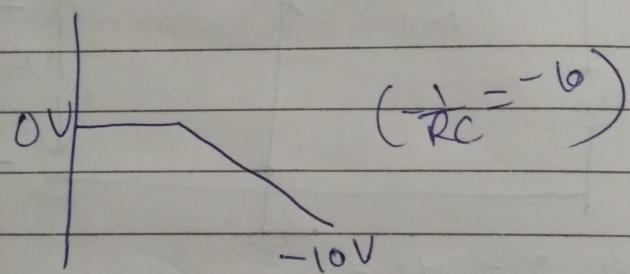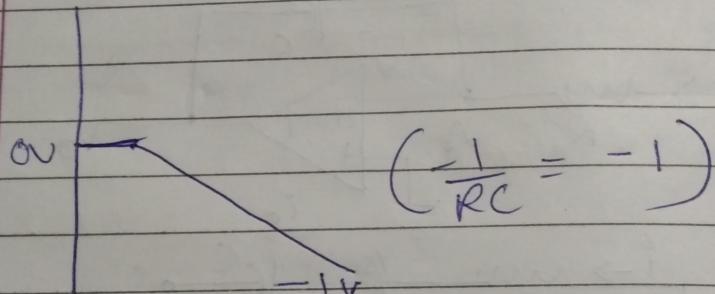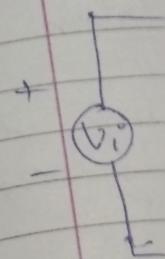

④ op-amp Differentiator :-

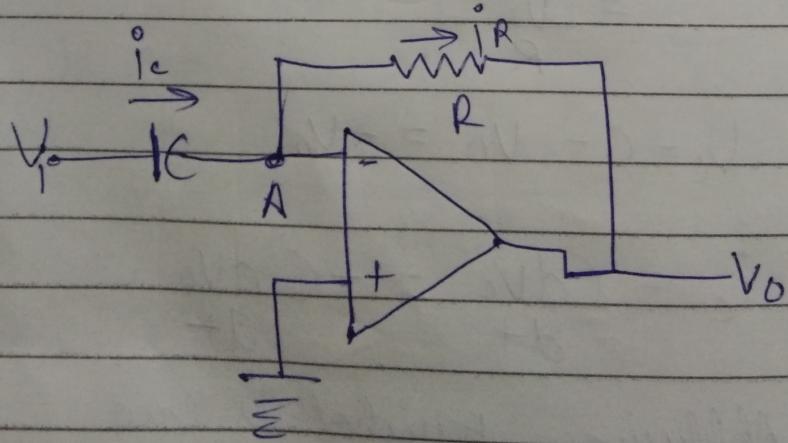

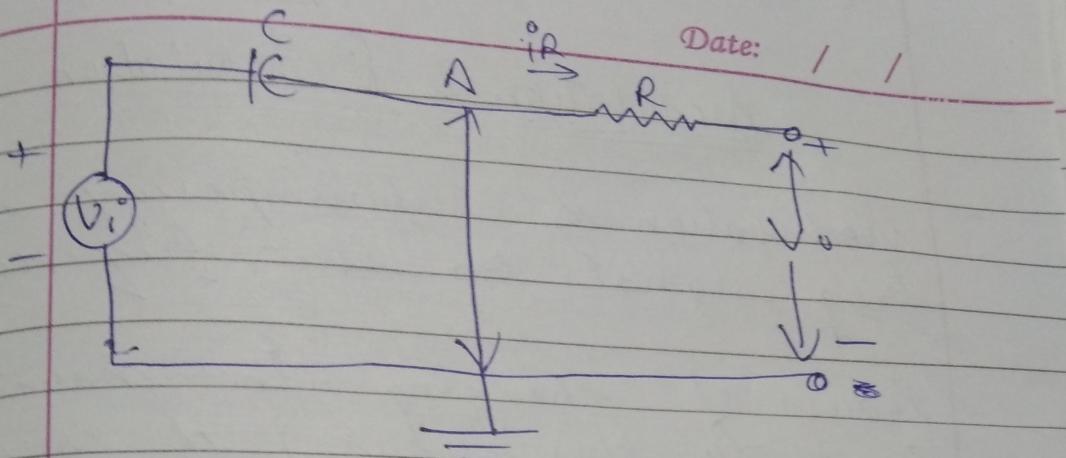



$$i_R = \frac{V_o - V_C}{R} = \frac{-V_o}{R} \quad \& \quad V_C = V_i - V_o = V_i$$

$$i_C = C \frac{dV_C}{dt} = C \frac{dV_i}{dt}$$

After K.C.L :-

$$-\frac{V_o}{R} = C \frac{dV_i}{dt} \quad (i_R = i_C)$$

$$V_o = -RC \frac{dV_i}{dt}$$

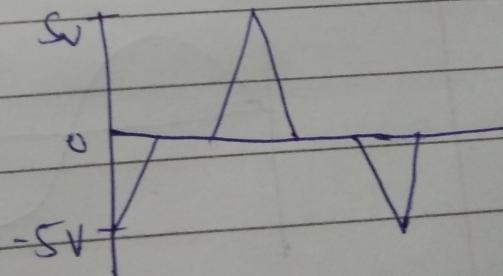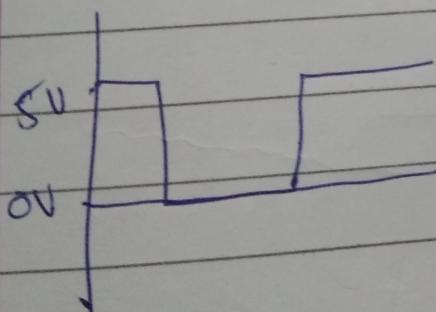

Date: / /

## Modulation & Demodulation

Modulation is superimposing low freq. signal on high freq. signal.

Process of changing some characteristics (amplitude, phase or freq.) of carrier wave in accordance with amplitude of signal is modulation.


- ① Reduce height of antenna

$$d = \frac{V}{f} = \frac{3 \times 10^8}{\text{freq. (Hz)}} \text{ meters}$$

- ② Operating range :-

- ③ Wireless communication.

- ④ Amplitude Modulation:-

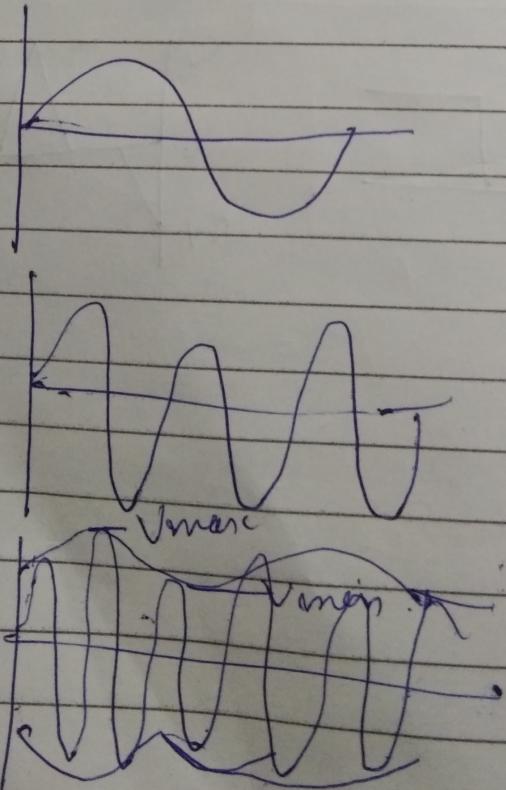

Date: / /

0  $m = \text{modulation index}$   
 $= \frac{V_{\max} - V_{\min}}{V_{\max} + V_{\min}}$

$m = 1$

$m > 0$  over modulate

$m < 1 - 0.5 \gamma$  No modulation.

### ★ Frequency Modulation :-

